

1. (17 %) For a MOS+BJT differential pair as shown in Fig. 1, the threshold voltage of NMOS  $M_1$  is 0.5 V and the thermal voltage for BJT  $Q_1$  is 25 mV. For  $Q_1$ , its  $V_{BE}$  is equal to 0.625 V when  $I_c = 100 \mu\text{A}$ . For the tail current source, let's assume it is an ideal one with 1 mA. Channel length modulation and Early effect can be neglected in calculation. Note that  $R_L = 0.5 \text{ K}\Omega$ .

 


Fig. 1

- (6 %) Please design the size of  $M_1$  and  $V_{in}$  such that both  $M_1$  and  $Q_1$  draw the same current. Note that  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$  and the voltage drop on current source is 200 mV.
- (6%) The design in part (a) yields an asymmetric pair. In order to design a fully differential circuit, the size of  $M_1$  and  $Q_1$  must be changed such that both  $M_1$  and  $Q_1$  have the same DC current bias and transconductance. Please calculate  $(W/L)_{M_1}$  and the number of  $Q_1$  in parallel.
- (5 %) Please calculate the differential gain in part (b).

2. (33 %) In Fig. 2, neglect body effect in all transistors. Note that  $(W/L)_{1,2} = 40/1$ ,  $(W/L)_{3,4} = 100/1$ ,  $\mu_n C_{ox} = 50 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 20 \mu\text{A}/\text{V}^2$ ,  $V_{An} = 100 \text{ V}$ ,  $|V_{Ap}| = 66.67 \text{ V}$ ,  $V_{in} = 0.5 \text{ V}$ , and  $V_{tp} = -0.5 \text{ V}$ .

 


Fig. 2

- (11 %) First, you can neglect the channel length modulation such that the amplifier gain is infinite. Then, for  $R_L = 75 \Omega$ , what is the minimum and maximum  $(W/L)_5$  such that all MOS transistors can operate in saturation region?
- (15 %) Now, let's choose  $(W/L)_5 = 3000$  and assume the internal node X has total equivalent capacitance 1 pF, what is the value of  $C_L$  (the total equivalent capacitance at  $V_{out}$ ) to maintain the phase margin at 45 degree? In this case, we would like to have  $V_{out}$  as the dominant pole. Also, please draw the small-signal model for this circuit.
- (7 %) Alternatively, we can design node X as the dominant pole. What is the maximum  $C_L$  in this case to keep phase margin better than 45 degree?

見背面

3. (25%) Given the quadrature oscillator circuit as shown below, answer the following questions.
- (5%) Show that the circuit involving the second OP amplifier is equivalent to a negative impedance converter, with equivalent impedance equal to  $-R_f$  when looking into the right of the node marked with  $v$ .
  - (5%) When  $R_f$  is equal to  $2R$ , show that the circuit at the right-hand-side of the output of the first OP amplifier acts as a non-inverting integrator.
  - (5%) Without considering the output limiter circuit, derive the loop gain of the entire circuit and hence calculate the frequency of oscillation.
  - (5%) Explain why the two output voltages at  $v_{O1}$  and  $v_{O2}$  have an exact phase difference of  $90^\circ$ .
  - (5%) Explain the function of the limiter circuit in sufficient detail (5%).

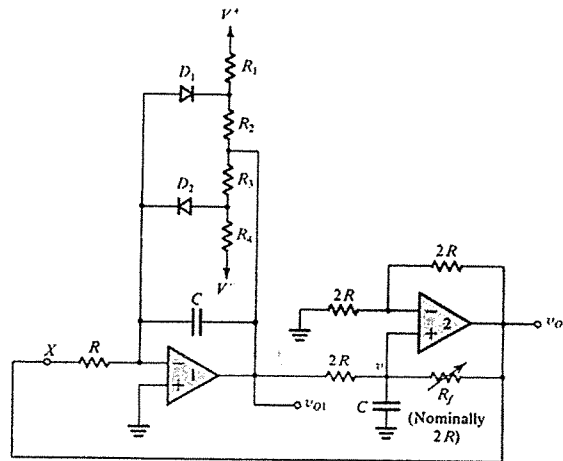


Fig. 3

接次頁

4. (25%) Given a static RAM cell based on the SR latch circuit shown in Fig.4a, the CMOS inverters are matched such that the circuit operation is symmetric around  $V_{DD}/2$ . Assume that the cell is storing a logic “0” in the output  $Q$ . A “set” operation by connecting  $S$  to voltage  $V_{DD}$  should ideally raise the voltage at the drain of  $Q_5$  to at least  $V_{DD}/2$  in order to trigger the regeneration via positive feedback. Here, assume for simplicity that the “set” operation involves only  $Q_2$  and  $Q_5$ , and at the end of the “set” operation the condition is like that shown in Fig.4b.

- (a) (5% each, total 10%) In what regions do the two transistors  $Q_2$  and  $Q_5$  operate?
- (b) (5%) List the equation that equals the drain currents of  $Q_2$  and  $Q_5$ .
- (c) (5%) For the “set” operation to successfully trigger the switch, what is the minimum  $W/L$  ratio of  $Q_5$  relative to  $Q_1$  (note: not relative to  $Q_2$ )?
- (d) (5%) For a 0.18- $\mu\text{m}$  fabrication process, with parameters  $\mu_n C_{ox} = 4 \mu_p C_{ox} = 300 \mu\text{A}/\text{V}^2$ ,  $V_{tn} = |V_{tp}| = 0.5 \text{ V}$ ,  $V_{DD} = 1.8 \text{ V}$ , plus the CMOS inverters  $(W/L)_n = 0.27 \mu\text{m}/0.18 \mu\text{m}$  and  $(W/L)_p = 4(W/L)_n$ , calculate  $(W/L)_5$  using a value at 1.5-fold of the minimum obtained from (c) for security.

 


Fig. 4a

 


Fig. 4b

試題隨卷繳回